



DEDAN KIMATHI UNIVERSITY OF TECHNOLOGY
UNIVERSITY EXAMINATIONS 2015/2016
SECOND YEAR SEMESTER II EXAMINATION FOR THE DEGREE OF BACHELOR OF SCIENCE IN
INFORMATION TECHNOLOGY

SPH 2172: PHYSICS

DATE: 22ND DECEMBER 2015

TIME: 1.30 PM – 3.30 PM

Some useful constants

- (1) Charge of an electron $e = 1.602 \times 10^{-19} C$
 (2) Speed of light $c = 3 \times 10^8 \text{ m/s}$
 (3) Permittivity of free space $= 8.854 \times 10^{-12} F/m$

INSTRUCTIONS


Answer questions one and any other two questions.

QUESTION ONE (30 MARKS)

- (a) State
- (i) Lenz's law. **(1 mark)**
- (ii) Kirchhoff's loop law. **(1 mark)**
- (b) Show that if three resistors are connected in parallel with resistance R_1, R_2 and R_3 then the total resistance R_T is given by $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$ **(4 marks)**
- (c) Determine the standard value of the carbon coded resistor
- Blue- violet- black- silver. **(2 marks)**
- (d) An alternating current is represented as $i = 120 \sin(\omega t)$. Calculate its $i_{r.m.s.}$ **(2 marks)**
- (e) An R-L a.c circuit is connected in series to 60 Hz 240 Vr.m.s supply. If the resistance is 120Ω and the inductance is 300mH, determine the circuit impedance. **(3 marks)**
- (f) A motor coil has 20Ω and 45Ω resistance when its temperature is $40^\circ C$ and $90^\circ C$ respectively. Find R_0 of the coil given that its temperature coefficient of resistance $\alpha = 0.0044/^\circ C$. **(4 marks)**
- (g) State two types of capacitors. **(2 mark)**
- (h) A certain station transmits its signals at 200km. Determine its frequency. **(3 marks)**
- (i) State and explain two ways how power loss can be reduced in a.c transmission. **(4 marks)**

- (j) Three charges are held fixed at the vertices of an equilateral triangle as shown below. Calculate their mutual electric potential energy (U). Take $q = 1.5 \times 10^{-5} C$ and $L = 70 \text{ cm}$. (4 marks)

+ 4q

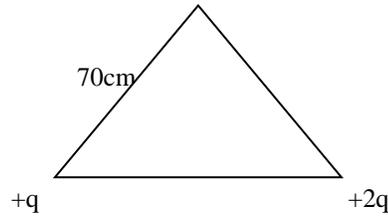


QUESTION TWO (20 marks)

- (a) For a purely inductive circuits show that the inductive reactance is given by $X_L = \omega L$ (5 marks)
- (b) A capacitor of $20 \mu F$ and resistor of 100Ω are connected in series across a $50 \text{ Hz } 230 V_{r.m.s}$ supply. Calculate
- (i) the impedance of the circuit. (3 marks)
 - (ii) the root mean square current. (2 marks)
- (c) Two signals $V_1 = 70 \sin(\omega t)$ and $V_2 = 90 \cos(\omega t)$ are fed into one circuit .Determine the representation of the superposed signal. (5 marks)
- (d) A particle having a charge $q = 5 \times 10^{-7} C$ moves from point P to point Q along a straight line, covering a distance of 6 m. The electric field is uniform along this line, in the direction from P to Q with magnitude $E = 600 \text{ N/C}$. calculate
- (i) the force on the charge. (3 marks)
 - (ii) the work done on it by the field. (2 marks)

QUESTION THREE (20 marks)

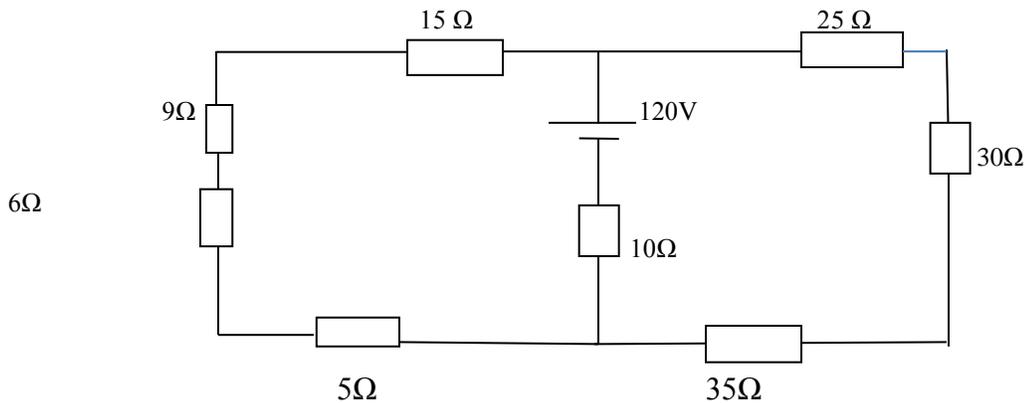- (a) Define the following terms.
- (i) electric current. (1 mark)
 - (ii) the potential (1 mark)
- (b) A certain circular conductor transmits a charge of $1200 C$ in 5 minutes. Given that the material making the conductor is 1.5 mm in diameter, calculate
- (i) The current in the wire . (3 marks)
 - (ii) its current density . (3 marks)
- (c) A straight wire 12 meters long carries a current of 2 A and is placed in a uniform magnetic field of $30 T$. Determine the force on the conductor if its inclined at 40° to the direction of the field. (3 marks)
- (d) Calculate the current in the circuit and the p.d across each resistor. (9 marks)



QUESTION FOUR (20 marks)

- (a) Define the following terms.
- (i) power . **(1 mark)**
 - (ii) electric field. **(1mark)**
- (b) A R-L d.c circuit consists a 100 mH inductor, a 20Ω resistor and a 24V d.c. The switch is closed at $t = 0$ seconds. Determine
- (i) the time constant of the circuit. **(2marks)**
 - (ii) the current in the circuit at $t = 2.5$ seconds. **(3marks)**
- (c) Two capacitor 4μF and 8μF are connected in parallel and the parallel connection is connected in series to 6μF capacitor .If the system is connected to 50V d.c ,determine
- (i) the total capacitance of the circuit. **(3 marks)**
 - (ii) the total charge stored by the circuit. **(2 marks)**
 - (iii)the energy stored in the circuit. **(3 marks)**
- (d)A parallel plate capacitor has two plates each of area of 25cm².It has a dielectric of 0.15mm thick and dielectric constant of 4.5.if the capacitor is connected across 12V d.c,calculate
- (i) Capacitance of the capacitor. **(3 marks)**
 - (ii) the flux density . **(2 marks)**

QUESTION FIVE (20 MARKS)

- (a) State and explain three factors that determine the resistance of a resistor. **(3 marks)**
- (b) State three factors that determine the induced e.m.f in self inductance. **(3 marks)**
- (c) Derive an expression of the electric potential energy U as a charge is moved from point r_a to r_b . **(4marks)**

(d) Determine the color coding of $34\text{ M}\Omega$ resistors having a tolerance a tolerance of $\pm 2\%$. **(3marks)**

(e) An a.c is represented as $V = 150 \sin (55\pi t + 3.5)$. Determine

- (i) the root mean square potential ($V_{r.m.s}$). **(2 mark)**
- (ii) the frequency and the period of the a.c. **(3 marks)**
- (iii) the value of the voltage at $t = 1.5$ seconds. **(2 marks)**