



UNIVERSITY EXAMINATION 2021/2022
THIRD YEAR SECOND SEMESTER EXAMINATION FOR THE DEGREE OF
BACHELOR OF SCIENCE IN ELECTRICAL AND ELECTRONIC ENGINEERING
&
BACHELOR OF SCIENCE IN TELECOMMUNICATION AND INFORMATION
ENGINEERING
&
BACHELOR OF EDUCATION IN TECHNOLOGY (ELECTRICAL AND ELECTRONIC
ENGINEERING)

EEE/ETI 3209: ANALOGUE ELECTRONICS II

DATE: JAN 2022

TIME: 2 HOURS

Instructions

This examination paper contains **FIVE** questions. Attempt **compulsory QUESTION ONE** and **any other TWO** questions.

QUESTION ONE (Compulsory)

- a) By use of sketches, discuss the difference between the following
 - i. CE, CB, CC **(3 Marks)**
 - ii. Saturation, Cutoff, Linear operation of an amplifier **(3 Marks)**
- b) Given $\beta = 200$ for both transistor Q1 and 2, determine the following
 - i. V_B, V_E, V_C, I_E . **(5 Marks)**
 - ii. Voltage gain at first and second (output) stage and output voltage V_o . **(5 Marks)**
 - iii. Overall gain and output voltage if a $1\text{ k}\Omega$ (R_L) is applied at the second stage **(3 Marks)**
 - iv. Calculate the input and output impedance and give suggestions on measures to be employed to reduce the mismatch. **(3 Marks)**

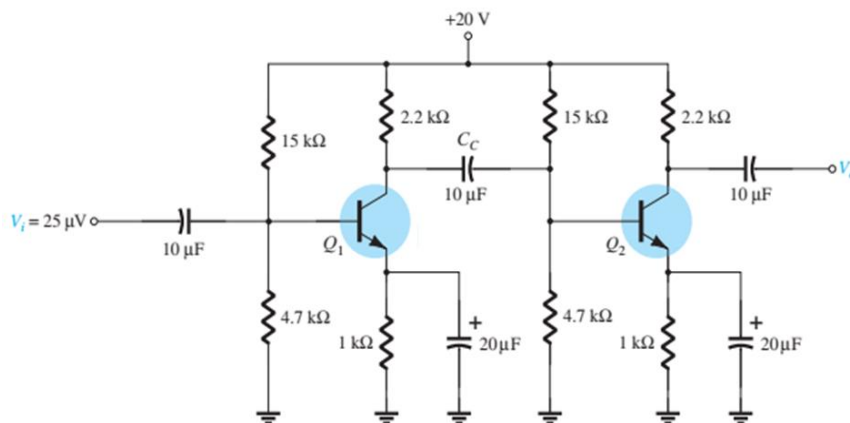


Fig. Q1.b

- c) An amplifier operating over the frequency range from 18 to 20 M Hz has a $10\text{ k}\Omega$ input resistor. Calculate the rms noise voltage at the input to this amplifier if the ambient temperature is 27°C **(4 Marks)**

- d) Briefly discuss the following amplifiers: Class A, Class B, Class AB and Class C (4 Marks)

QUESTION 2

- a) A circuit has these values: $\beta_{DC} = 200$, $R_C = 1.0 \text{ k}\Omega$, $V_{CC} = 24 \text{ V.}$, $V_{BB} = 10 \text{ V.}$, $R_B = 47 \text{ k}\Omega$
- Draw circuit (1 Mark)
 - Find the Q-point (3 Marks)
 - Draw the load line (3 Marks)
 - Determine the maximum peak value of base current for linear operation (3 Marks)
- b) Starting from the RC circuit shown in Fig. 2b, derive the equations necessary for low frequency response to prove the relation $A_v(\text{dB}) = -20 \log_{10} (f_L/f)$ (10 Marks)

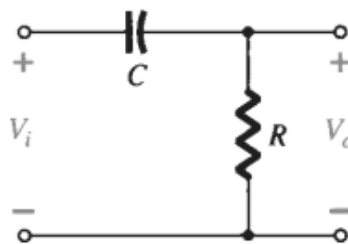


Fig. Q2b

QUESTION 3

- a) Determine the cut-off frequencies for the network shown in Fig 3a using the following parameters $C_s = 10 \text{ }\mu\text{F}$, $C_E = 20 \text{ }\mu\text{F}$, $C_C = 1 \text{ }\mu\text{F}$, $R_1 = 40 \text{ k}\Omega$, $R_2 = 10 \text{ k}\Omega$, $R_L = 2.2 \text{ k}\Omega$, $R_E = 2 \text{ k}\Omega$, $R_C = 4 \text{ k}\Omega$, $\beta = 100$, $r_o = \infty \Omega$, $V_{CC} = 20 \text{ V}$ (10 Marks)

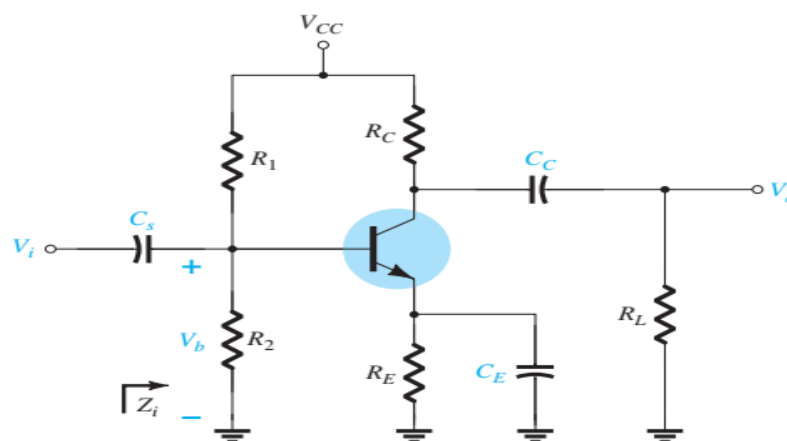


Fig Q3(a)

- b) Repeat the analysis of 3a above with a source resistance R_s of $1 \text{ k}\Omega$ and comment on the effects of internal series resistance on gain and operating bandwidth. (10 Marks)

QUESTION 4

- a) In the circuit shown in Fig. 4a below, $A_v(\text{mid})$ gain = -90, $r_e = 15.8 \Omega$, $C_{be} = 36 \text{ pF}$, $C_{bc} = 4 \text{ pF}$, $C_{ce} = 1 \text{ pF}$, $C_{Wi} = 6 \text{ pF}$, $C_{Wo} = 8 \text{ pF}$, $C_s = 10 \text{ uF}$, $C_E = 20 \text{ uF}$, $C_C = 1 \text{ uF}$, $R_1 = 40 \text{ k}\Omega$, $R_2 = 10 \text{ k}\Omega$, $R_L = 2.2 \text{ k}\Omega$, $R_E = 2 \text{ k}\Omega$, $R_C = 4 \text{ k}\Omega$, $h_{fe} = 100$, $r_o = \infty \Omega$, $V_{CC} = 20 \text{ V}$

- i. Determine f_{Hi} and f_{Ho} **(7 Marks)**
- ii. Find f_B and f_T **(3 Marks)**

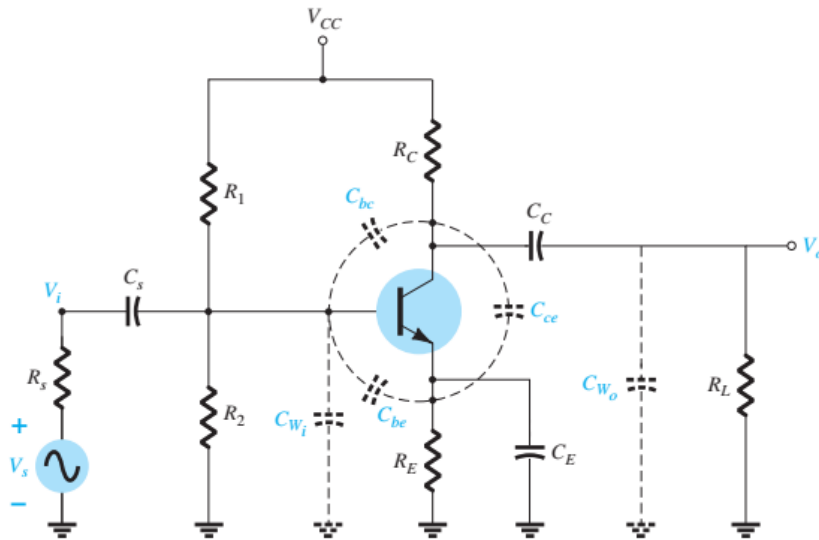


Fig Q4a

- b) A certain diff-amp has a differential voltage gain of 2000 and a common-mode gain of 0.2. Determine the CMRR in dB **(2 Marks)**
- c) By use of bode plots, explain octave and decade as applied in transistors **(3 Marks)**
- d) A class C amplifier with $V_{CC} = 24 \text{ V}$ and $R_C = 100 \Omega$ is driven by a 200 kHz signal. The transistor is on for 1 μs , and the amplifier is operating over 100% of its load line. If $I_{c(\text{sat})} = 100 \text{ mA}$ and $V_{ce(\text{sat})} = 0.2 \text{ V}$;
 - i. What is the average power dissipation of the transistor **(2 Marks)**
 - ii. The efficiency of the amplifier **(3 Marks)**

QUESTION 5

- a) The circuit of Fig. Q5a has an input of 12 V rms
 - i. Identify the type of amplifier **(1 Mark)**
 - ii. Calculate the input and output power **(5 Marks)**
 - iii. Efficiency of the amplifier and compare it with ideal performance **(1 Marks)**

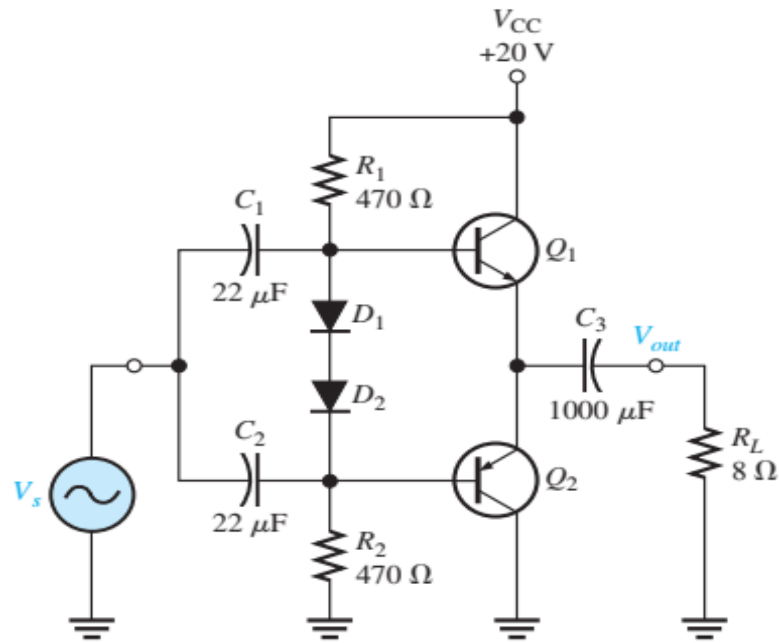


Fig. Q5a

b) For circuit shown in Fig. Q5b,

- i. Calculate the relevant dc and ac parameters (5 Mark)
- ii. Calculate the current, voltage and power gain (5 Mark)

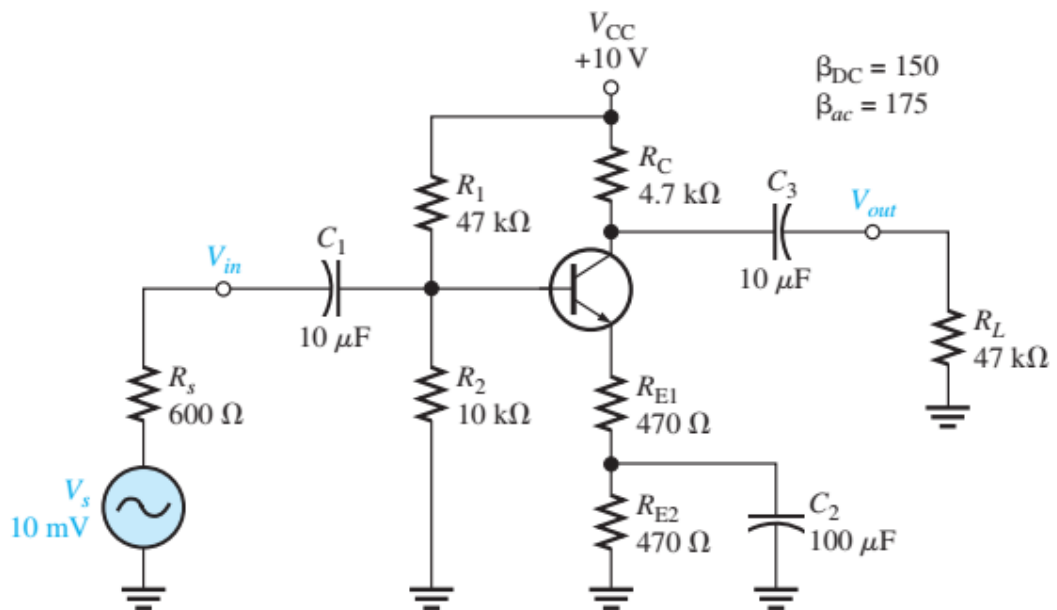


Fig. Q5b

- c) Determine the noise figure in dB of an amplifier for which the noise equivalent resistance $R_{eq} = 2.5 \text{ k}\Omega$ and $R_t = 600 \text{ }\Omega$ if the driving generator has an output impedance of $50 \text{ }\Omega$ (Large mismatch). (3 Mark)