



DEDAN KIMATHI UNIVERSITY OF TECHNOLOGY  
SUPPLEMENTARY/SPECIAL UNIVERSITY EXAMINATIONS –  
2020/2021

FIRST YEAR SUPPLEMENTARY/SPECIAL EXAMINATION FOR THE  
DEGREE OF BACHELOR OF SCIENCE IN ELECTRICAL AND  
ELECTRONIC ENGINEERING, BACHELOR OF EDUCATION IN  
TECHNOLOGY (ELECTRICAL AND ELECTRONIC) ENGINEERING,  
AND BACHELOR OF SCIENCE IN TELECOMMUNICATION AND  
INFORMATION ENGINEERING

EEE & TIE 1202: CIRCUIT NETWORK THEORY

DATE: OCTOBER 2021

TIME: 2 Hours

---

**INSTRUCTIONS**

This paper consists of **FIVE** questions. Answer questions **ONE** and **ANY OTHER TWO**.

**QUESTION ONE**

**30 marks**

- a) Explain the two general approaches to network analysis giving examples

6 marks

- b) Given the circuit (Fig 1b) and  $J=5$  A;  $E_0=20$  V;  $R_1=4$   $\Omega$ ;  $R_2=2.4$   $\Omega$ ;  $R_3=1.6$   $\Omega$ ;  $R_4=6$   $\Omega$ ., Find the values of all currents

6 marks

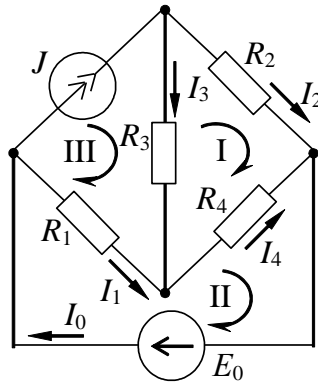


Fig. 1b

c) Explain the Kirchoff's first and second law

6 marks

d) The equation of an alternating current is given by  $i = 42.42 \sin 628t$ . Calculate its i) Maximum value ii) Frequency iii) RMS value iv) Average Value v) Form Factor.

5 marks

e) Write the polar form of voltage given by,  $V = 100 \sin \left( 100\pi + \frac{\pi}{6} \right) V$

2 marks

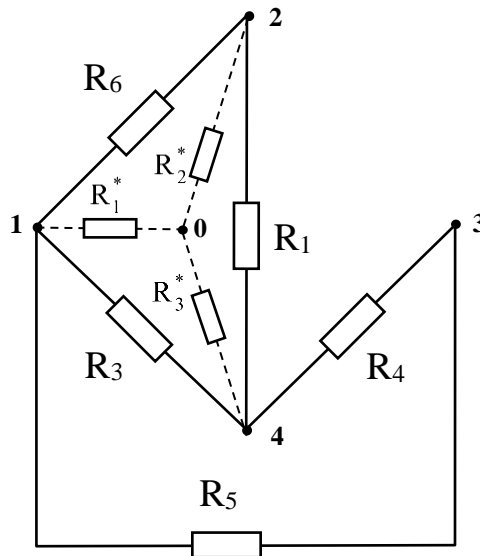


Fig. 1f

f) Transform delta resistances  $R_1, R_3, R_6$  to star resistances  $R_1^*, R_2^*, R_3^*$ : (see fig 1f) and then solve for equivalent resistance given that  $R_1 = R_4 = 5 \Omega, R_3 = R_6 = 4 \Omega, R_5 = 3 \Omega,$


5 marks

**QUESTION TWO**

**20 marks**

a) Given the circuit parameters of circuit Fig 2a as:  $R_1 = R_4 = 5 \Omega, R_2 = R_3 = R_6 = 4 \Omega, R_5 = 3 \Omega, R_7 = 6 \Omega, E_1 = 42 V, E_2 = 50V, E_3 = 40V, E_4 = 60V, E_5 = E_7 = 20V, I = 4 A$

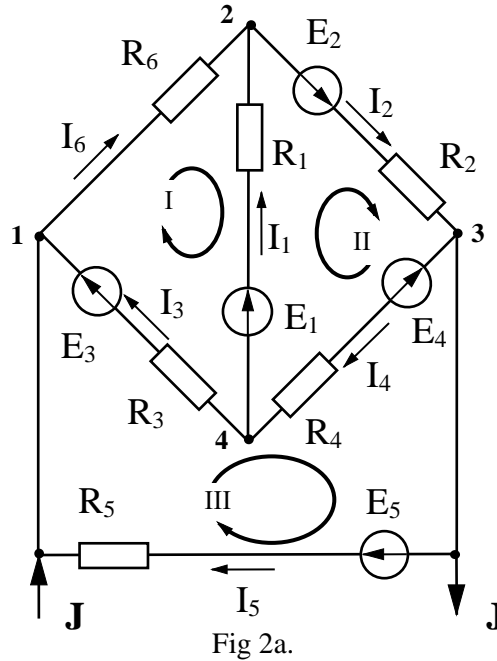- i. Write the system equation according to Kirchhoff's Current law for node 1, 2, and 3. 2 marks
- ii. Write the system equation according to Kirchhoff's Voltage Law for loop 1, loop 2, and loop 3. 3 marks
- iii. Find the value of all currents using the current loop method. 10 marks



- b) Two a.c. Voltages are represented by:  $v_1(t) = 30 \sin(314t + 45^\circ)$ ,  $v_2(t) = 60 \sin(314t + 60^\circ)$ , Calculate the resultant voltage  $v(t)$  and express in the form  $v(t) = V_m \sin(314t + \phi)$ , 5 marks

### QUESTION THREE

**20 marks**

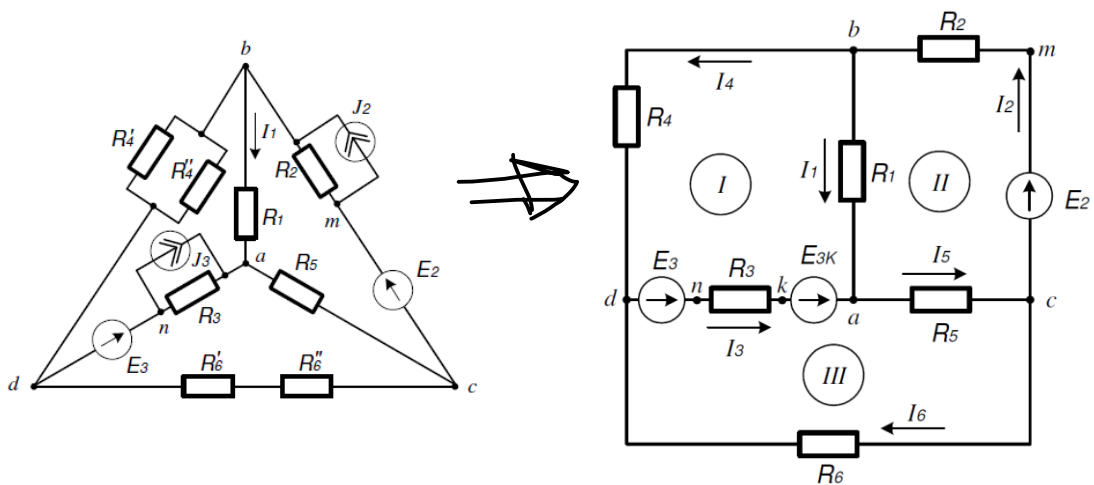


Fig 3a.

- a) Given that, the circuit parameters:  $R_1 = 20 \Omega$ ,  $R_2 = 80 \Omega$ ,  $R_3 = 100 \Omega$ ,  $R'_4 = 70 \Omega$ ,  $R''_4 = 70 \Omega$ ,  $R'_6 = 24 \Omega$ ,  $R''_6 = 16 \Omega$ ,  $R_5 = 150 \Omega$ ,  $E_2 = 100V$ ,  $E_3 = 150V$ ,  $I_2 = 0 A$ ,  $I_3 = 1 A$ , find the value of all currents ( $I_1$  to  $I_6$ ) using Nodal method where reference node is taken as  $V_d$  (fig 3a).

16 marks

- b) Write 4 ways of representing a.c. Voltage, given by a magnitude of 5V and frequency 50 Hz.

4 marks

**QUESTION FOUR**

**20 marks**

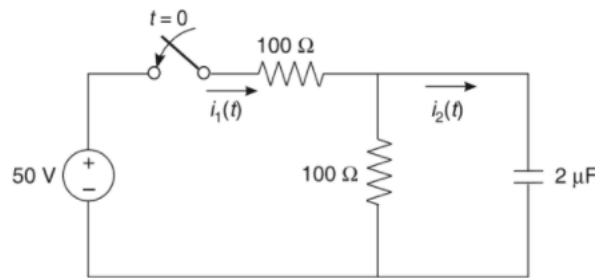


Fig 4a.

- a) Solve for  $I_1(t)$  and  $I_2(t)$  in the circuit shown when the switch is closed at  $t=0$ , using the Laplace Transformation method (fig 4a)

15 marks

- b) Find the current  $I_1$ ,  $I_2$ , and  $I_3$  shown in the circuit (fig.4b), If  $V=120 B$ ,  $R_1=18 \Omega$ ,  $R_2=30 \Omega$ ,  $R_3=2 \Omega$ .

5 marks

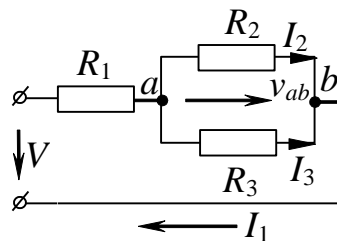


Fig 4b.

**QUESTION FIVE**

**20 marks**

- a) Find the values of currents in the circuit (Fig 5a) using the Nodal method given that  $E_1=20V$ ,  $E_2=24 V$ ,  $E_3=12 V$ ,  $R_1=R_3=R_4=2 \Omega$ ,  $R_2=8 \Omega$ ,  $R_5=R_6=4 \Omega$ . And taking  $\phi_1=0$  (reference node)

8 marks

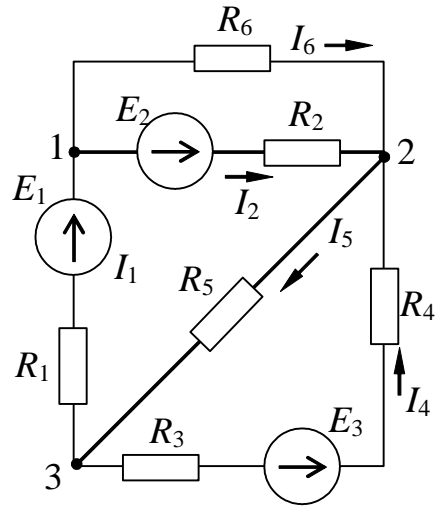


Fig 5a.

- b) For Fig 5b, Let the switch be closed at  $t=0$  so that the series RL circuit is excited by the DC voltage  $V$ . Find the equation for the current using the Classical method.

8 marks

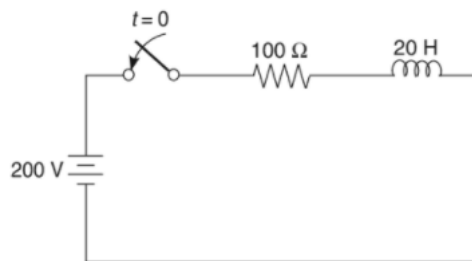


Fig 5b.

- c) Discuss the steps to achieve Thevenin equivalent circuit.

4 marks